

ACTIVITY SHEET


Name:

Hand in instructions:

A SIMPLE SERIES CIRCUIT



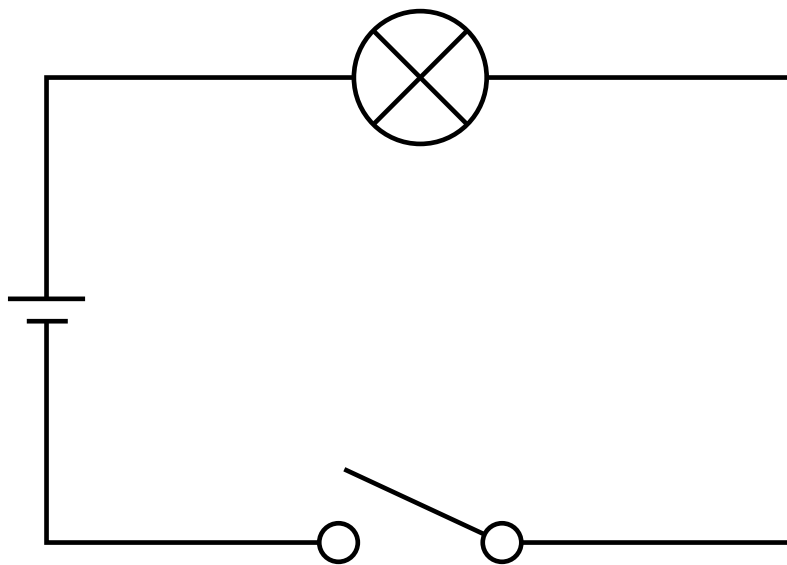Here's an example of a simple series circuit:



YOUR CHALLENGES

1

Write the name of each component next to its symbol.

2

Circle the component you'd use to control the flow of electricity.

3

Indicate the positive and negative points of the power source.

For more info and inspirational resources, visit
drax.com/resources/educational-resources

